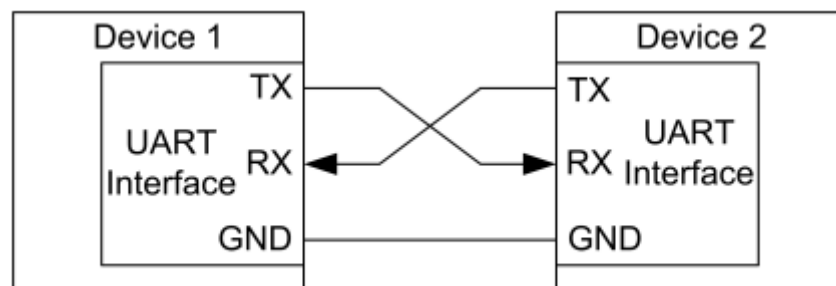



# UART Receiver
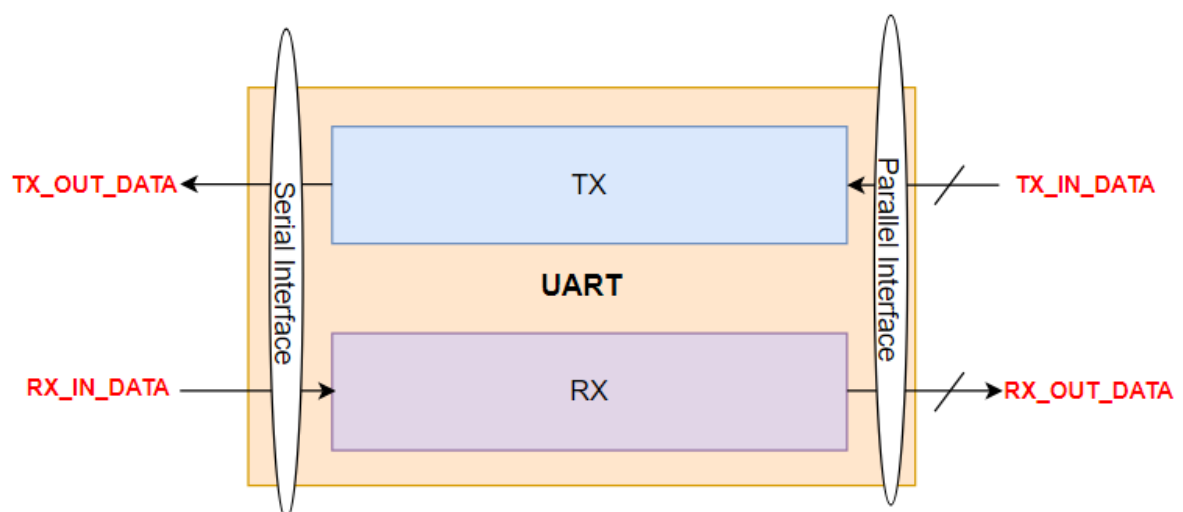
## Introduction: -


- There are many serial communication protocols as I2C, UART and SPI.
- A **U**niversal **A**synchronous **R**eceiver/**T**ransmitter (UART) is a block of circuitry responsible for implementing serial communication.
- UART is Full Duplex protocol (data transmission in both directions simultaneously)



- **Transmitting UART** converts parallel data from the master device (eg. CPU) into serial form and transmits in serial to the receiving UART.
- **Receiving UART** will then convert the serial data back into parallel data for the receiving device.



**Block Interface: -**

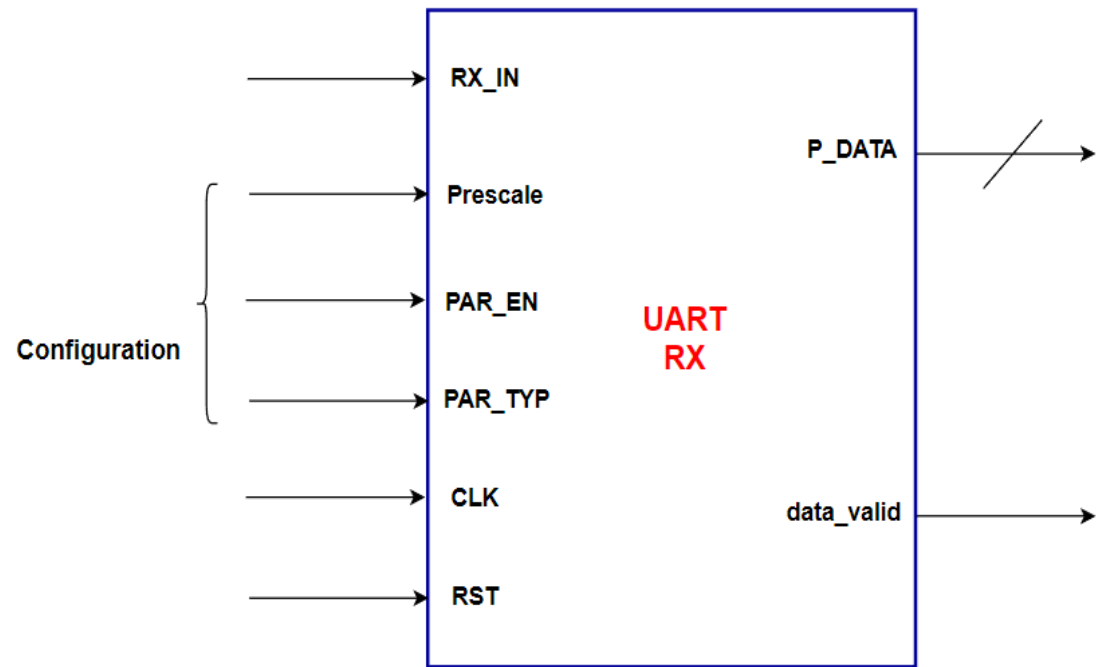

| Port       | Width | Description               |
|------------|-------|---------------------------|
| CLK        | 1     | UART RX Clock Signal      |
| RST        | 1     | Synchronized reset signal |
| PAR_TYP    | 1     | Parity Type               |
| PAR_EN     | 1     | Parity_Enable             |
| Prescale   | 6     | Oversampling Prescale     |
| RX_IN      | 1     | Serial Data IN            |
| P_DATA     | 8     | Frame Data Byte           |
| Data_valid | 1     | Data Byte Valid signal    |


## Specifications: -

- UART RX receive a UART frame on **RX\_IN**.
- UART\_RX support **oversampling** by 8, 16, 32
- **RX\_IN** is high in the **IDLE** case (No transmission).
- **PAR\_ERR** signal is **high** when the calculated parity bit not equal the received frame parity bit as this mean that the frame is corrupted.
- **STP\_ERR** signal is **high** when the received stop bit not equal 1 as this mean that the frame is corrupted.
- DATA is extracted from the received frame and then sent through **P\_DATA** bus associated with **DATA\_VLD** signal **only** after checking that the frame is received correctly and not corrupted. (PAR\_ERR = 0 && STP\_ERR = 0).
- **UART\_RX can accept consequent frames without any gap.**
- Registers are cleared using asynchronous active low reset
- **PAR\_EN (Configuration)**
  - 0: To disable frame parity bit
  - 1: To enable frame parity bit
- **PAR\_TYP (Configuration)**
  - 0: Even parity bit
  - 1: Odd parity bit

## All Expected Received Frames: -

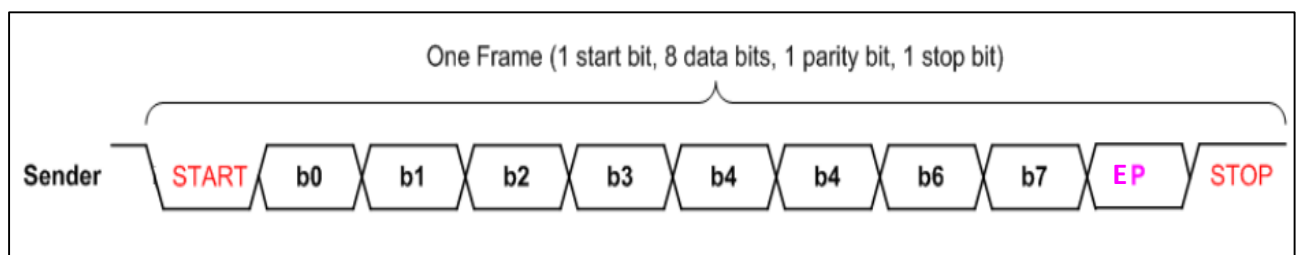
### 1. Data Frame (**in case of Parity is enabled & Parity Type is even**)

- One start bit (1'b0)
- Data (LSB first or MSB, 8 bits)
- Even Parity bit
- One stop bit



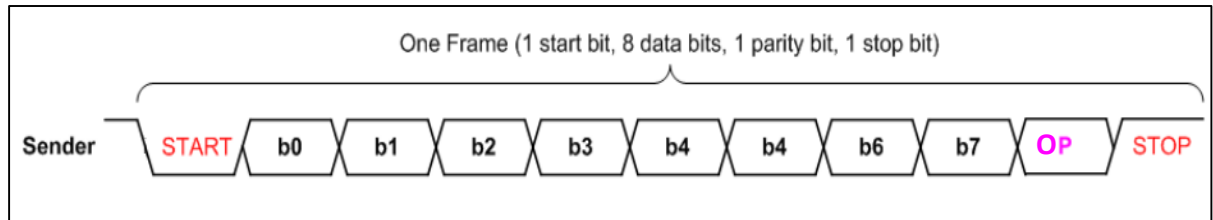
## 2. Data Frame (in case of Parity is enabled & Parity Type is odd)

- One start bit (1'b0)
- Data (LSB first or MSB, 8 bits)
- Odd Parity bit
- One stop bit


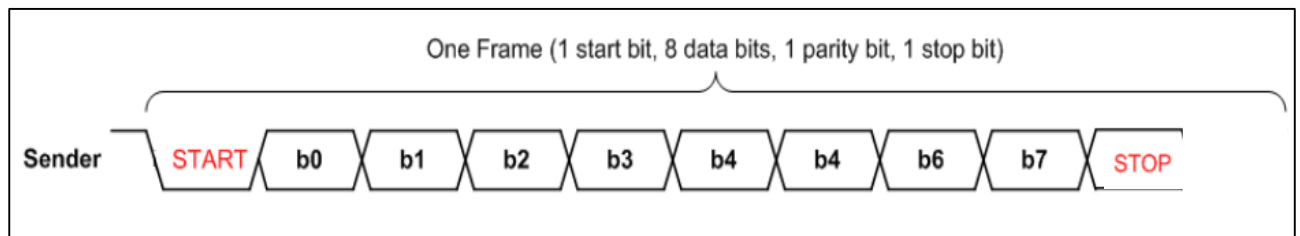
## 3. Data Frame (in case of Parity is not Enabled)


- One start bit (1'b0)
- Data (LSB first or MSB, 8 bits)
- One stop bit



## Waveforms: -

### Expected Input (RX\_IN): -


#### 1. In case of one frame: -

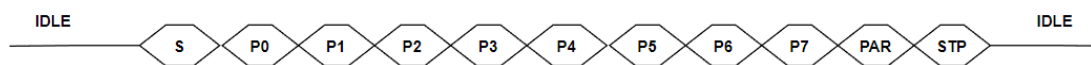

#### 2. In case of consequent frames: -




### Expected Output: -

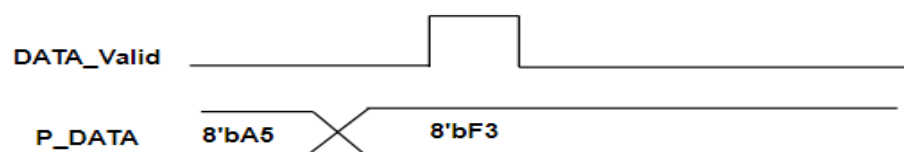


## Oversampling: -

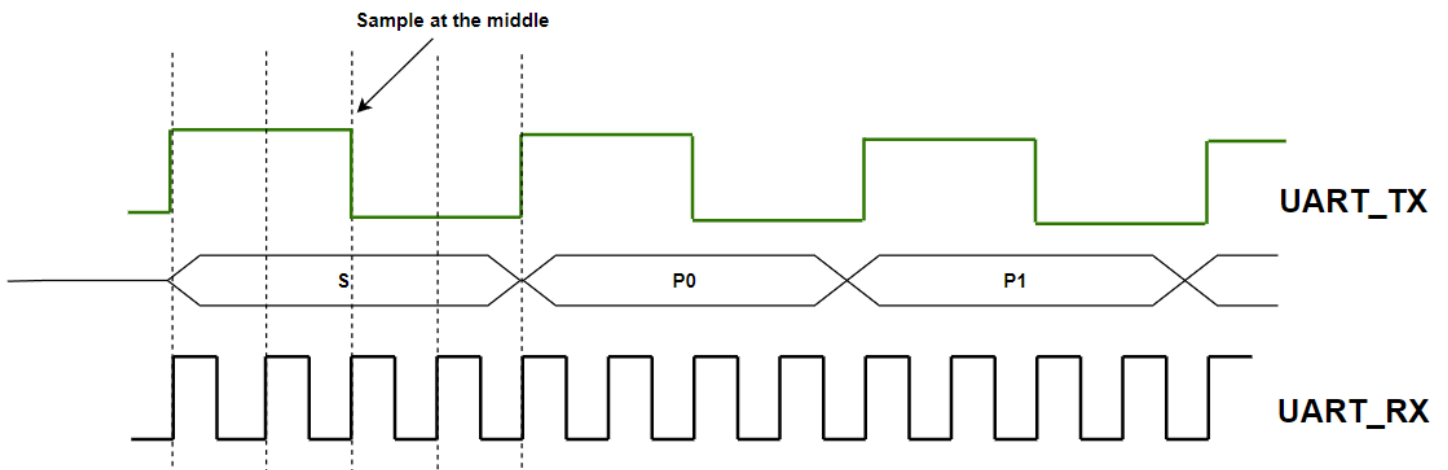**1. Oversampling by 4: This means that the clock speed of UART\_RX is 4 times the speed of UART\_TX.**




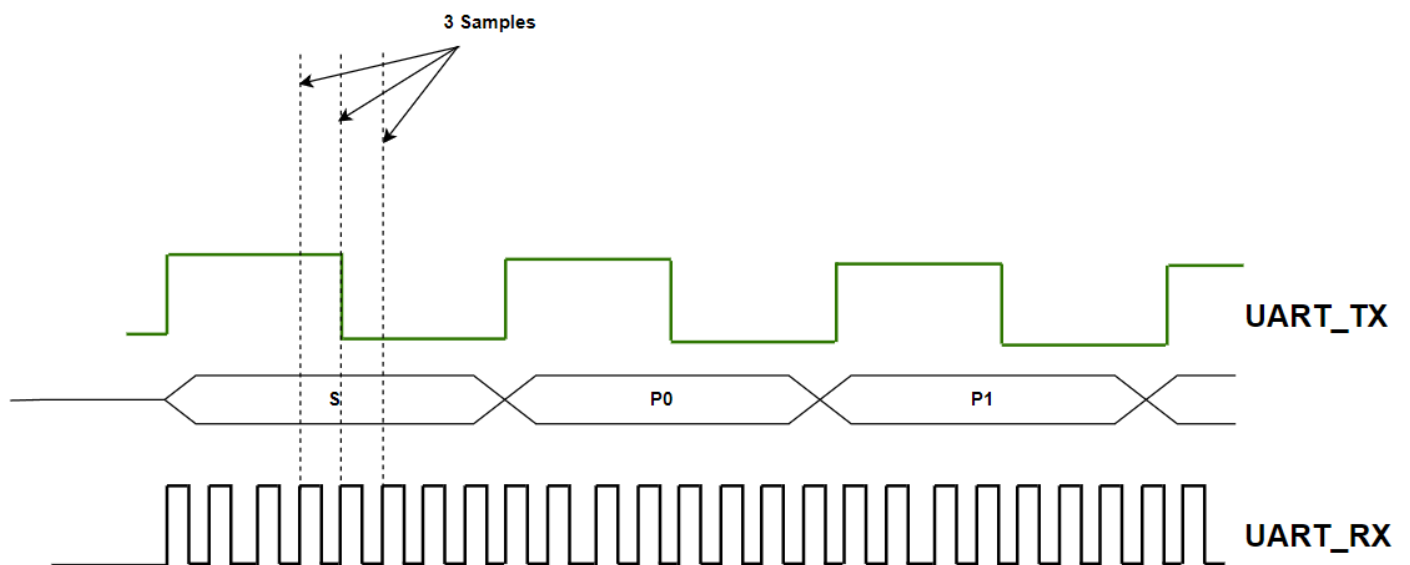**2. Oversampling by 8: This means that the clock speed of UART\_RX is 8 times the speed of UART\_TX.**



we will mainly use prescaler 16

## Recommended Block Diagram: -

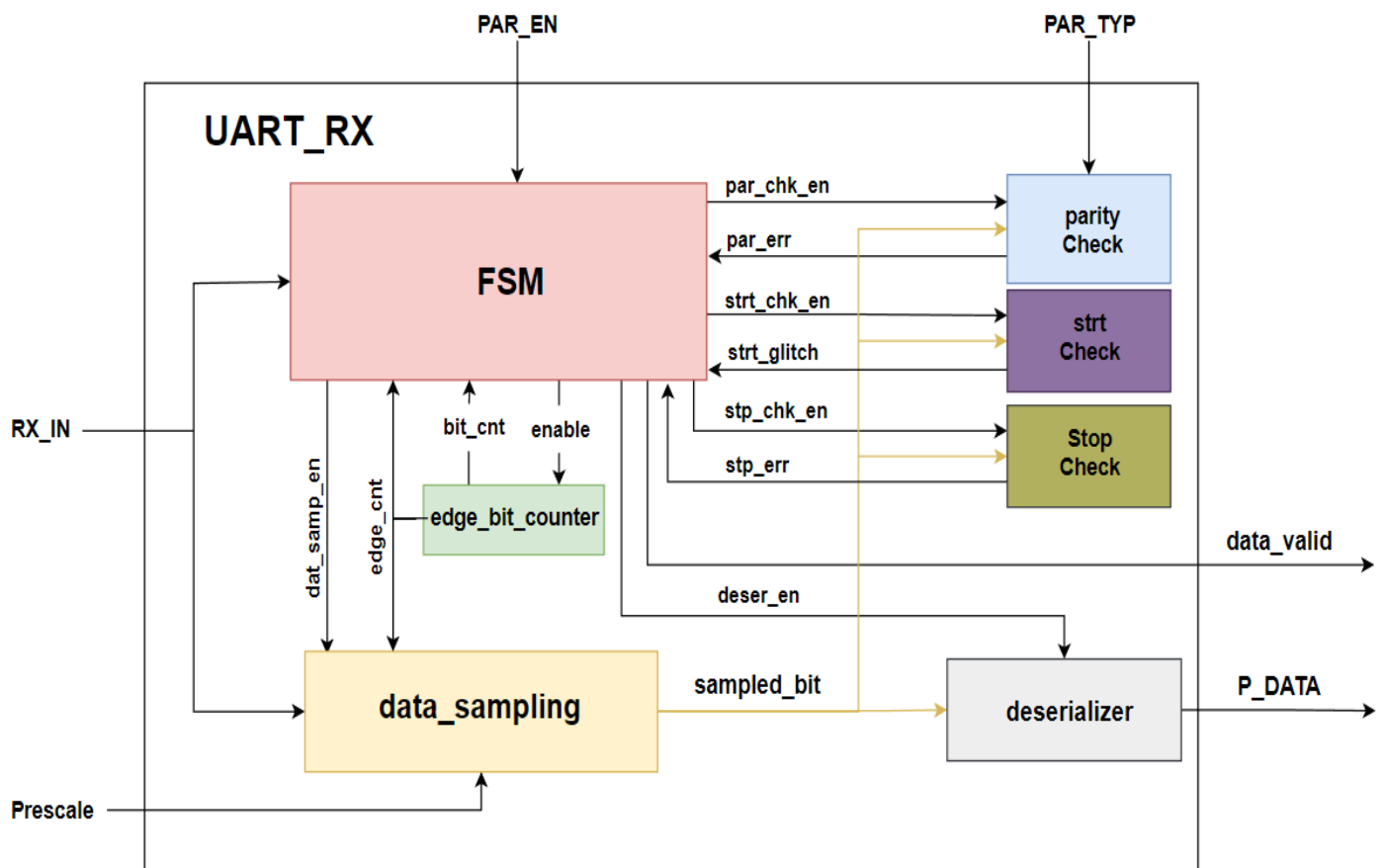

## Requirements: -

- 1- Implement the above Specifications for UART RX using Verilog language.
- 2- Write a testbench to validate your design using 200 MHz clock frequency.